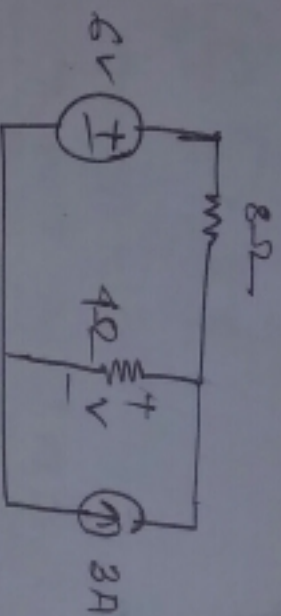


Super position Theorem: The current through or voltage drop in any elements of a network is equal to the algebraic sum of the currents or voltages produced independently by each source.


Ex:



Find V ?

Solⁿ:

When 6V is active:

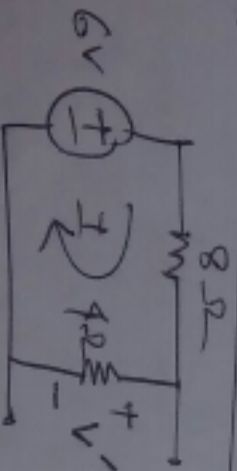


$$6V - 8I - 4I = 0$$

$$\Rightarrow I = 6/12 = 0.5A$$


$$\therefore V' = 4 \times 0.5 = 2V$$

When 3A active:

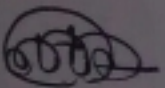


$$\therefore I_4 = \frac{8}{8+4} \times 3 = 2A$$

$$\therefore V'' = 2 \times 4 = 8V$$

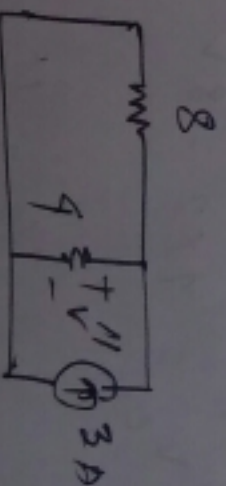


$$\therefore V = V' + V'' = -10V$$

(2)

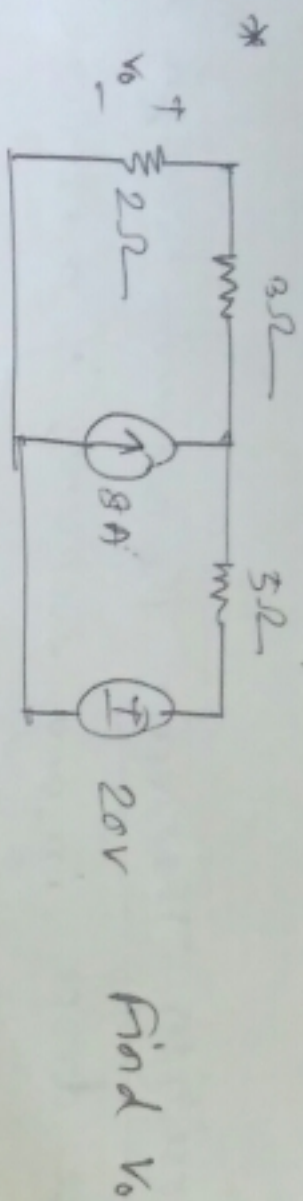

Solⁿ:

When, 20V active

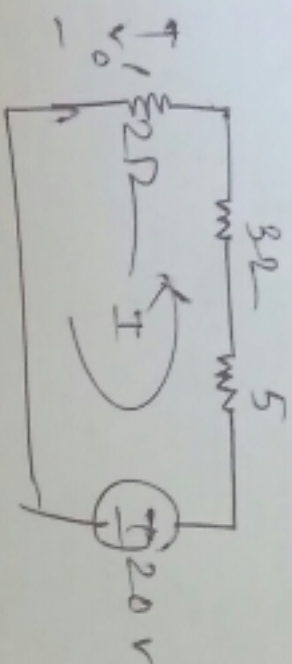


$$20 - (5 + 3 + 2)I = 0$$

$$\Rightarrow I = \frac{20}{10} = 2A$$

$$\therefore V_o' = 2 \times 2 = 4V$$


When 8A active:

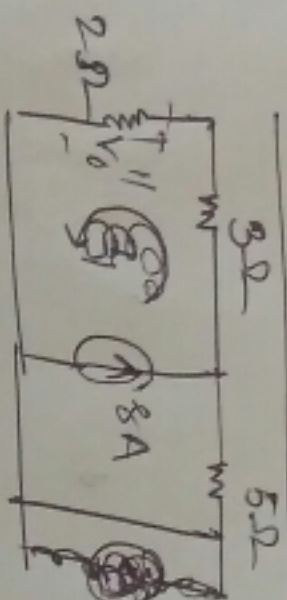

$$\therefore I_{2\Omega} = \frac{5}{5 + (3 + 2)} \times 8 = \frac{40}{10} = 4$$

$$\therefore V_o'' = 4 \times 2 = 8V$$
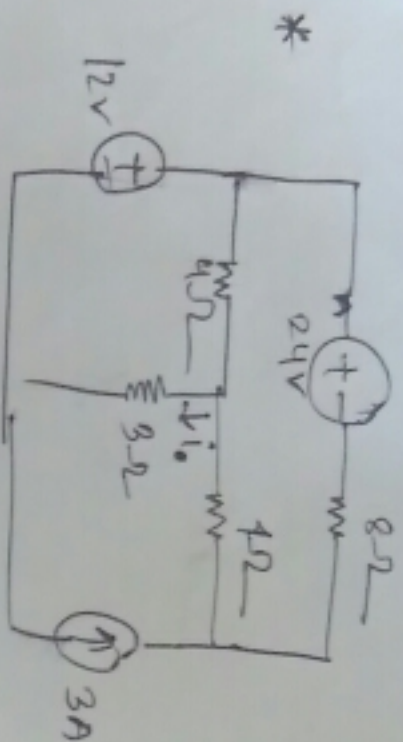
$$\therefore V_o = V_o' + V_o'' = 4 + 8 = 12V$$



Find i using
superposition thm.

Solⁿ:

When 12V active:



using KVL at loop-1

$$12 - 4I_1 + 4I_2 - 3I_1 = 0$$

$$\Rightarrow 7I_1 - 4I_2 = 12 \quad \text{--- (I)}$$


using KVL at loop-2

$$-(8+4)I_2 - 4(I_2 - I_1) = 0$$

$$\Rightarrow 4I_1 - 16I_2 = 0$$

$$\Rightarrow I_1 - 4I_2 = 0$$

When 24V active:

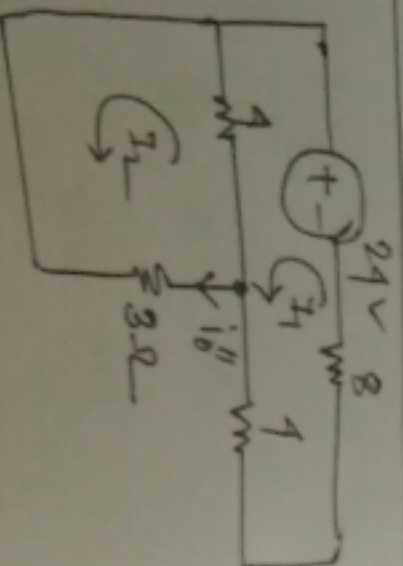

using KVL at loop-1

$$24 - 4(I_1 - I_2) - 12I_1 = 0$$

$$\Rightarrow 4I_1 - I_2 = 6$$

using KVL at loop-2

$$4(I_2 - I_1) - 3I_2 = 0$$

$$\Rightarrow 4I_1 - 7I_2 = 0$$

From (I) & (II)

$$I_1 = 2A$$

$$I_2 = \frac{1}{2}A$$

$$\therefore i' = 2A$$




$$\therefore I_1 = 1.75$$

$$I_2 = 1$$

$$\therefore I_0'' = -I_2 = -1$$

When, 3 A active:

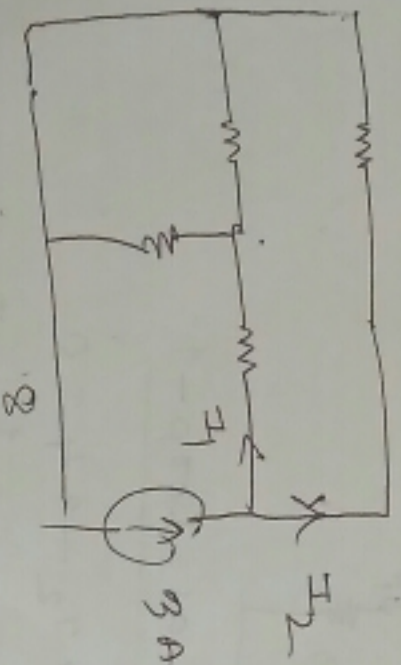


$$\therefore I_1 = \frac{4}{(4 + 3) + 1} \times 3 = 1.75$$

$$\therefore I_0'' = \frac{4}{3 + 4} \times 1.75 = \frac{7}{4} = 1.75$$

$$\therefore I = I_0'' + I_0''' = 1.75 + 0.25 = 2A$$


Ex: (superposition)

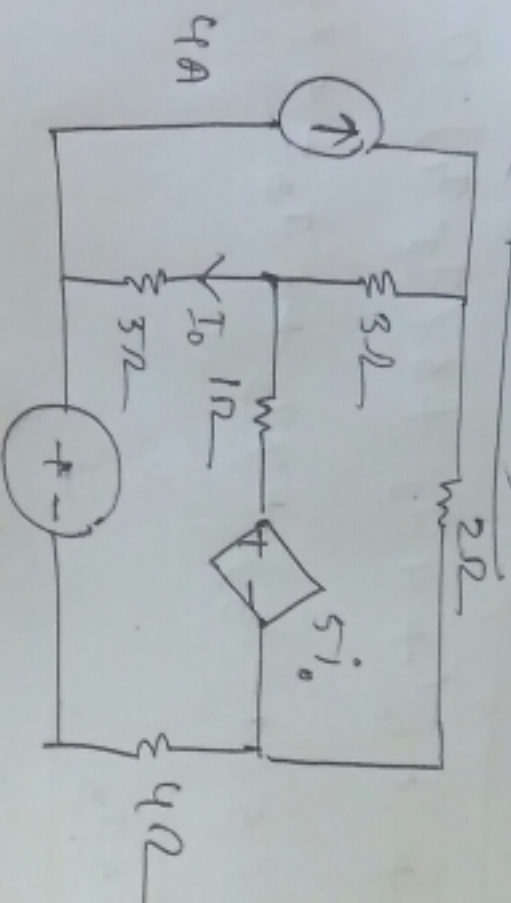

Find I_o ?

Soln:

when, 4A active:

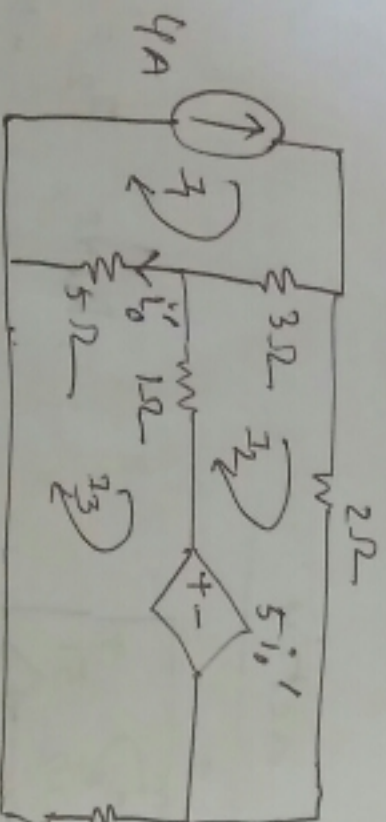

here,
 $I_1 - I_2 = i_o$

$$\Rightarrow i_o = 4 - I_3$$

Applying KVL at loop-2

$$2I_2 - 5i_o + 3(I_2 - I_3) + 3(I_2 - I_1) = 0$$

$$\Rightarrow 2I_2 - 5(4 - I_3) + 3(4 - I_3) + 3I_2 - 3 \times 4 = 0$$

$$\Rightarrow 6I_2 + 4I_3 = 92$$

$$\Rightarrow \boxed{3I_2 + 2I_3 = 46}$$

$$\boxed{3I_2 + 2I_3 = 16}$$

KVL at loop-3

$$(I_3 - I_2) + 5I_0' + 4I_3 + 5(I_3 - I_1) = 0$$

$$\Rightarrow I_3 - I_2 + 5(4 - I_3) + 4I_3 + 5I_3 - 5 \times 4 = 0$$


$$\Rightarrow \boxed{-I_2 + 5I_3}$$

$$\therefore I_1 = 80/70$$

$$I_2 = 16/17$$

$$\therefore I' = 4 - I_3 = 4 - 16/17 = 52/17 \text{ A}$$

When, no v active:

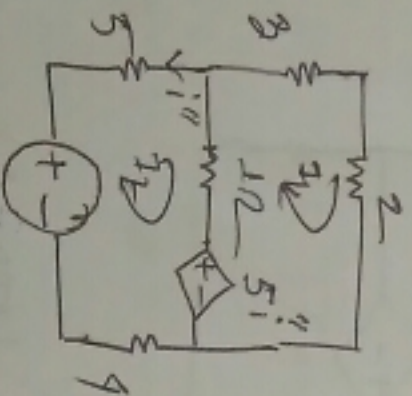

$$\text{Here, } I_2 = -I_0' \\ \Rightarrow I_0'' = -I_2$$

KVL at loop-1

$$2I_1 - 5I_0'' + (I_1 - I_2) + 3I_1 = 0$$

$$\Rightarrow 2I_1 + 5I_2 + I_1 - I_2 + 3I_1 = 0$$

$$\Rightarrow 6I_1 + 4I_2 = 0$$

$$\Rightarrow -3I_1 + 2I_2 = 0$$

KVL at loop-2

$$(I_2 - I_1) + 5I_0'' + 4I_2 - 20 + 5I_2 = 0$$

$$\Rightarrow I_2 - I_1 - 5I_2 + 4I_2 + 5I_2 - 20 = 0$$


$$\Rightarrow -I_1 + 5I_2 = 20$$

$$\therefore I_1 = -40/17, I_2 = 60/17$$


$$\therefore I_0'' = -60/17$$

$$\therefore I_0 = 52/17 - 60/17 = -8/17 \text{ (Ans)}$$

when, not active:

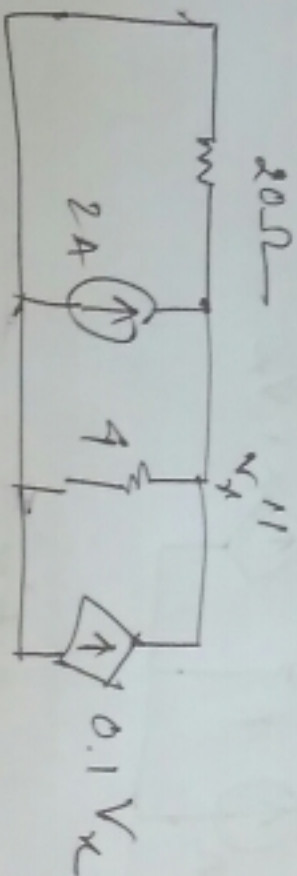

using KCL at node -

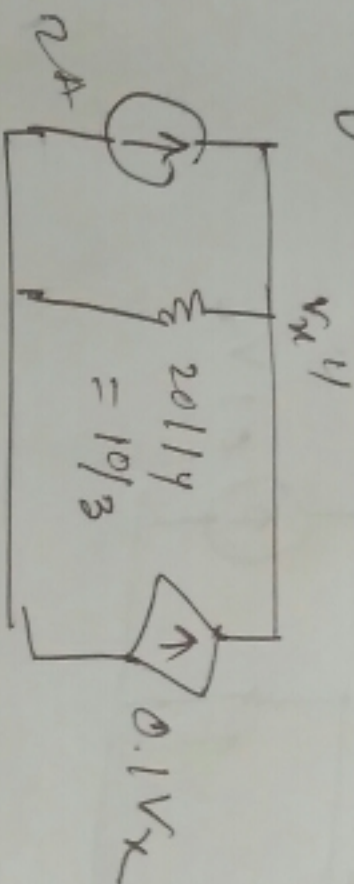

using KCL at node

$$2 + 0.1V_x'' = \frac{V_x''}{10/3}$$


$$\Rightarrow 2 + 0.1V_x'' = 0.3V_x''$$

$$\Rightarrow 0.2V_x'' = 2$$

$$\Rightarrow V_x'' = 10$$


$$\therefore V_x = V_x' + V_x'' = 2.5 + 10 = 12.5 \text{ V}$$

Ex. (super position)

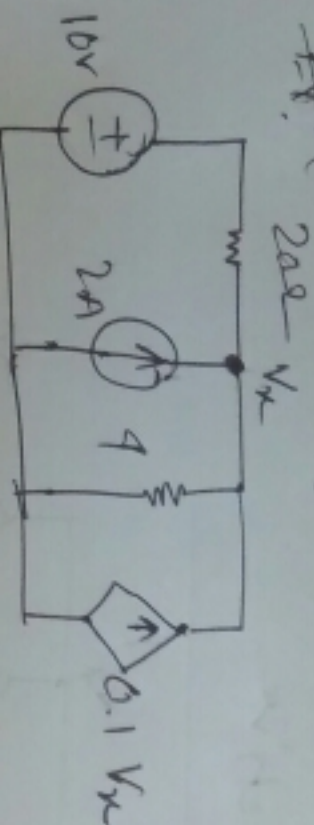

Find V_x ?

10V, 10V active:

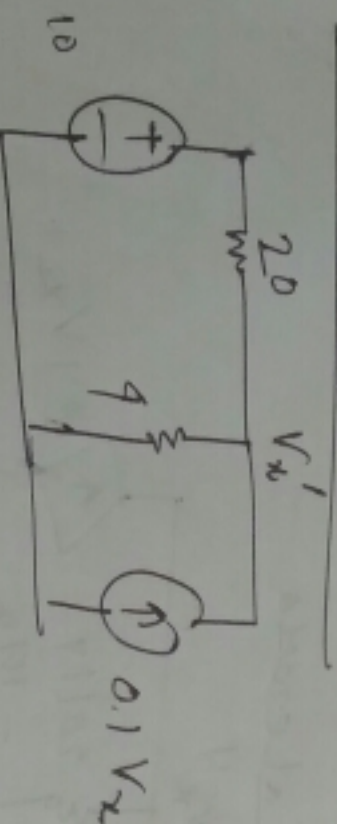

using KCL

$$\frac{10 - V_x'}{20} + 0.1 V_x' = \frac{V_x'}{4}$$

$$\Rightarrow \frac{10 - V_x'}{20} + 0.1 V_x' - \frac{V_x'}{4} = 0$$

$$\Rightarrow \frac{10 - V_x' + 2 V_x' - 5 V_x'}{20} = 0$$

$$\Rightarrow -4 V_x' = -10$$

$$\Rightarrow V_x' = 2.5$$