

**EEE 421**  
**Microprocessor and**  
**Interfacing**

# **Chapter 9**


## **Digital Interfacing**

# **Programmable Parallel Ports and Handshake Input/output**

# Methods of parallel Data Transfer

 
## □SIMPLE INPUT AND OUTPUT:

- This method is applied to get digital data from a simple switch like thermostat, into a microprocessor.
- Example:
  - ✓ connect the switch to an input port line and read the port.
  - ✓ connect the input of the LED buffer on an output.


 
# Methods of parallel Data Transfer

- SIMPLE STROBE I/O:
- In many applications, valid data is present on an external device only at a certain time, so it must be read in at that time. For Example: ASCII keyboard.
- The sending device, such as a keyboard, output parallel data on the data lines, and then outputs an STB signal to let you know that valid data is present.





# Methods of parallel Data Transfer

- For low rates of data transfer, such as from a keyboard to microprocessor this method is suitable.
- However, for higher speed data transfer this method does not work, because there is no signal which tells the sending device when it is safe to send the next data byte.

# Methods of parallel Data Transfer
 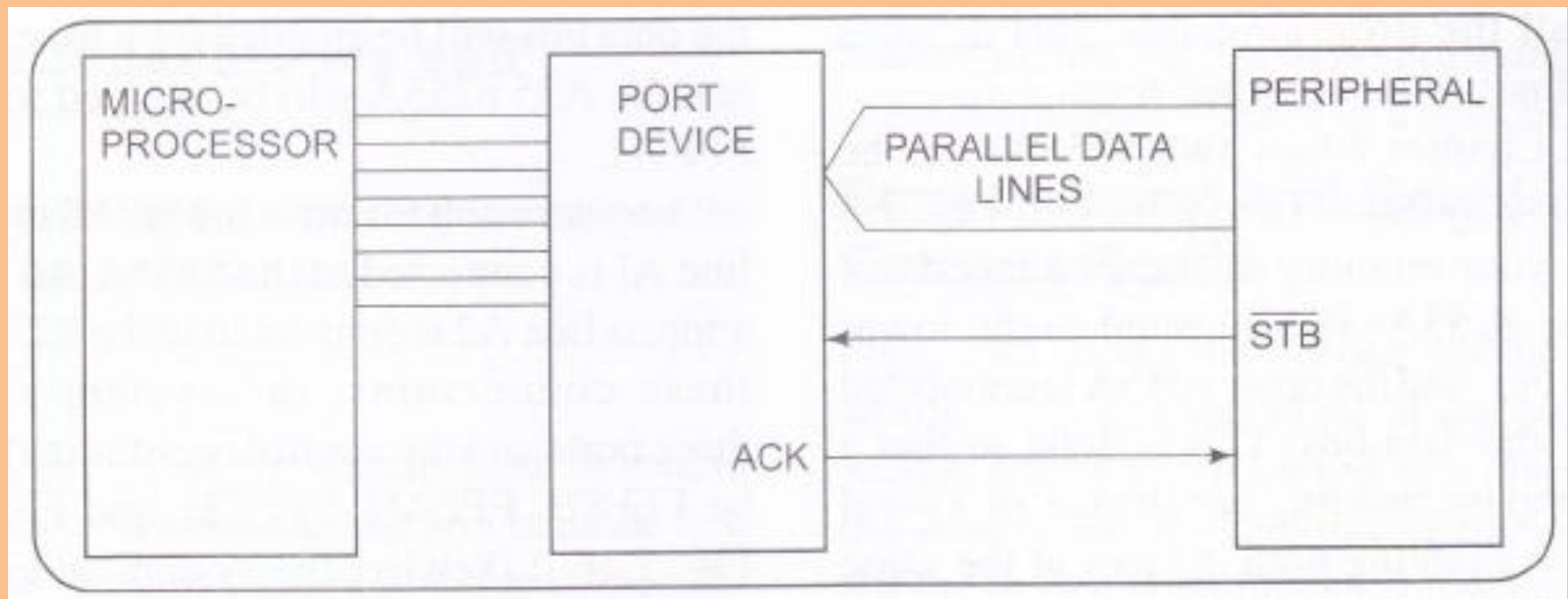
## □ SINGLE HANDSHAKE I/O:

- The peripheral outputs some parallel data and sends an STB signal to the microprocessor. The microprocessor detects the asserted  $\overline{\text{STB}}$  signal on a polled or interrupt basis and reads in the bytes of data.
- Then the microprocessor sends an Acknowledge signal (ACK) to the peripheral to indicate that the data has been read and that the peripheral can send the next byte of data.






# Methods of parallel Data Transfer
 
## ❑ Double Handshake Data Transfer


- ❖ Used in more coordinated system.
- ❖ STB low: Are you ready?
- ❖ ACK high: I am ready.
- ❖ The peripheral then send data
- ❖ STB high: some valid data for peripheral.
- ❖ ACK low: I have the data,



# Implementing Handshake data transfer

- 8255 is a port device ,which can be programmed to manage  $\overline{STB}$  and ACK signal in proper time.

# 8255 internal Block Diagram

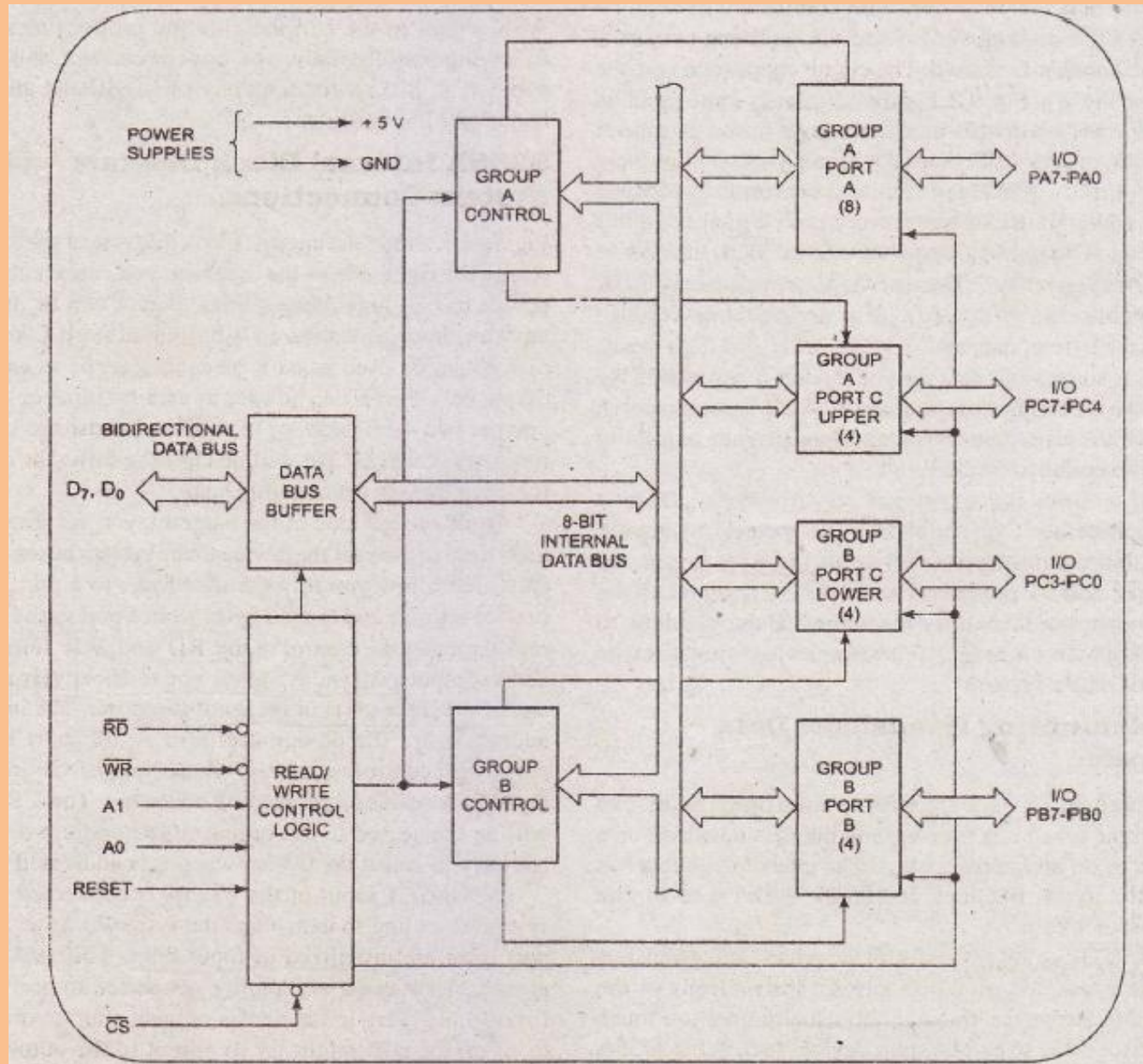

# 8255 Pin Configuration

- Port A ,B can be used in 8 bit input or output.
- Port C can be used in 8 bit input or output  
or
- Two 4 bit input or output port  
or
- Produce hand shake signal for port A or B.
- $\overline{WR}$  allows to write in port or status register.
- $\overline{RD}$  allows to read from port or status register.
- A0-A1:select address
- A1A0= 00:Port A
- A1A0= 01:Port B
- A1A0= 10:Port C
- A1A0= 11:Control Register

# 8255 Pin Configuration

- $\overline{\text{CS}}$ : helps to enable chip at specified address.
- RESET: connected to system reset. When system is reset, All ports are initialized as input to prevent destruction of circuitry.
- 7.8 (Sheet 5) the addresses are
- Port A: FFF8H
- Port B: FFFAH
- Port C: FFFCH
- Control Register: FFFE H

# 8255 Operation Modes and Initialization

## ❑ *Mode 0:*

- Both port A and B are normally initialized and no handshake.
- Port C is used 8 bit port or independent two 4 bit port.




## ❑ *Mode 1:*

- Both port A or port B can be used as handshake (strobed) input or output operation.
- Pins PC0, PC1, and PC2 function as handshake lines for port B if it is initialized in mode 1.
- Pins PC3, PC4 and PC5 function as handshake lines for port A if it is initialized as input port in mode 1.
- Pins PC6 and PC7 are available for use as input lines or output lines.
- If port A is initialized as a handshake output port, then port C pins PC3, PC6 and PC7 function as handshake signals.
- Port C pins PC4 and PC5 are available for use as input or output lines.

# 8255 Operation Modes and Initialization

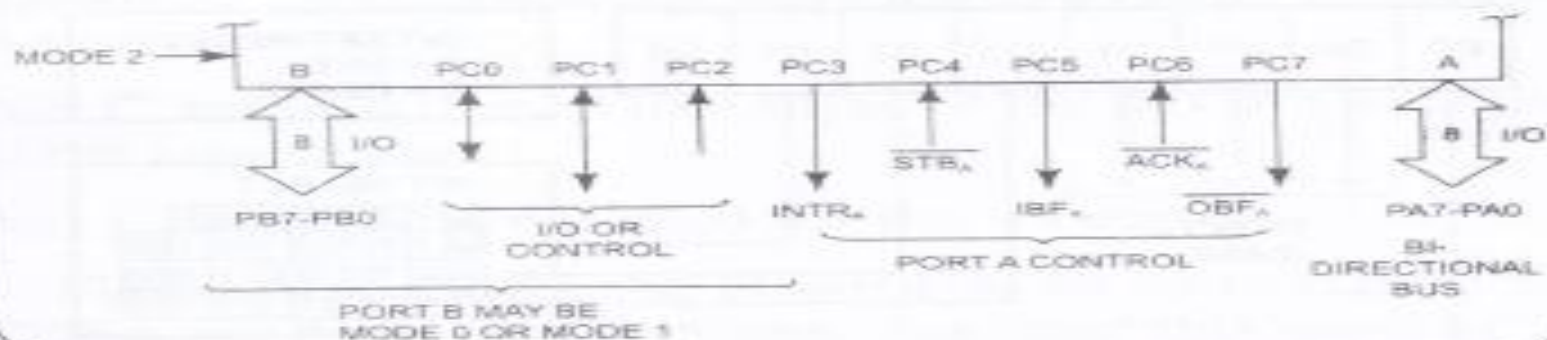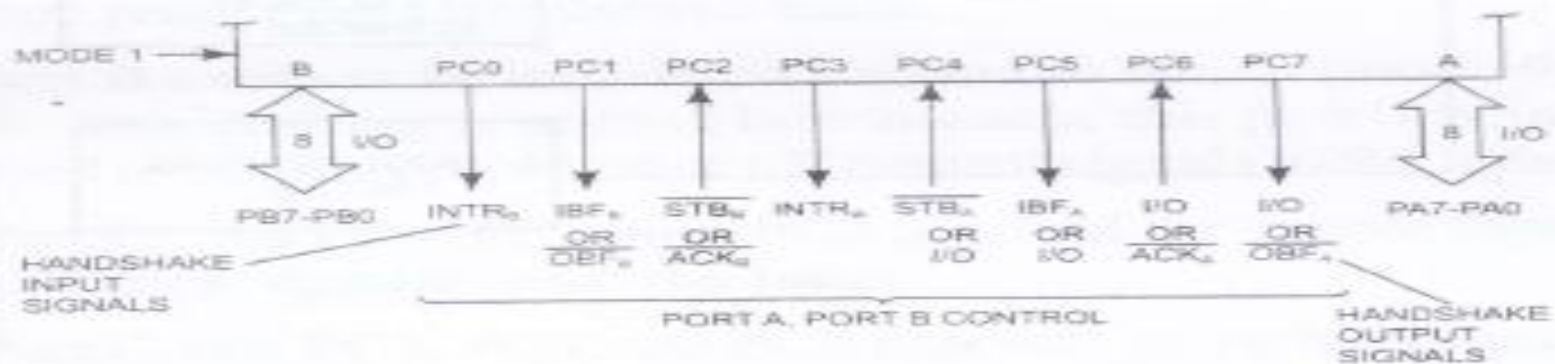
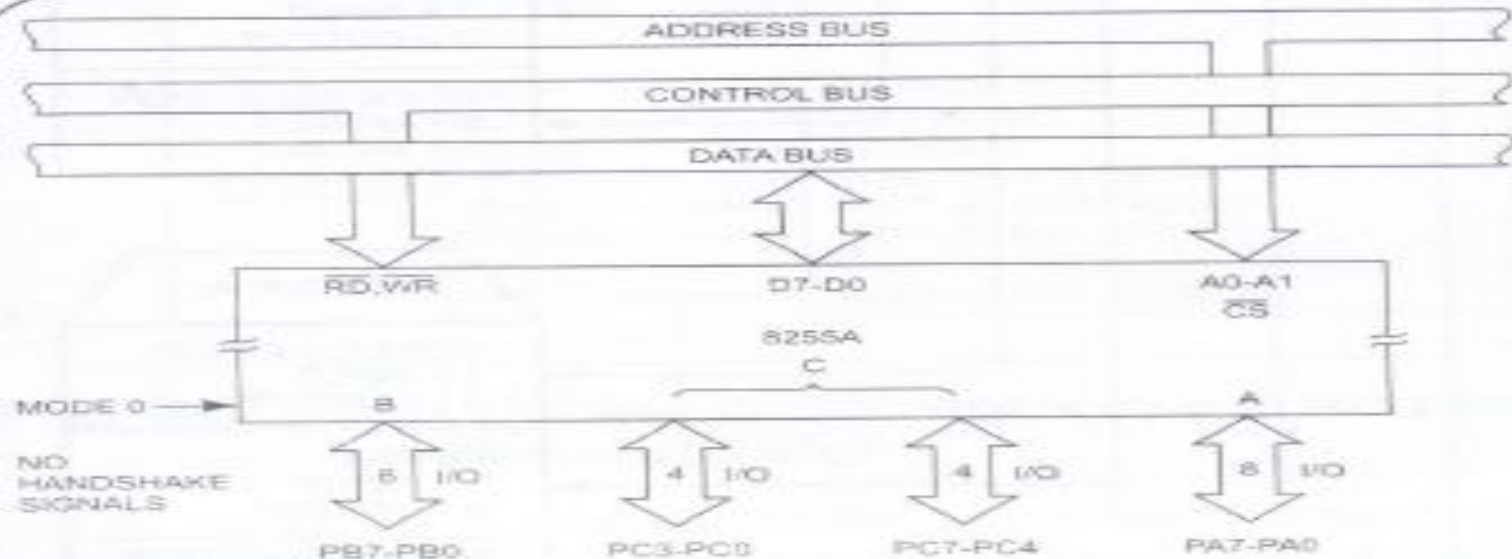
## □ *Mode 2:*

- Only port A can be initialized in mode 2 and bidirectional handshake data transfer.
- if port A is initialized in mode 2, then pins PC3 to PC7 used as handshake lines for port A.
- The other three pin PC0 to PC2 used as I/O port if port B is in mode 0.
- The three pins will be used for port B handshake lines if port B is initialized in mode 1.





# Constructing and Sending 8255A Control Words

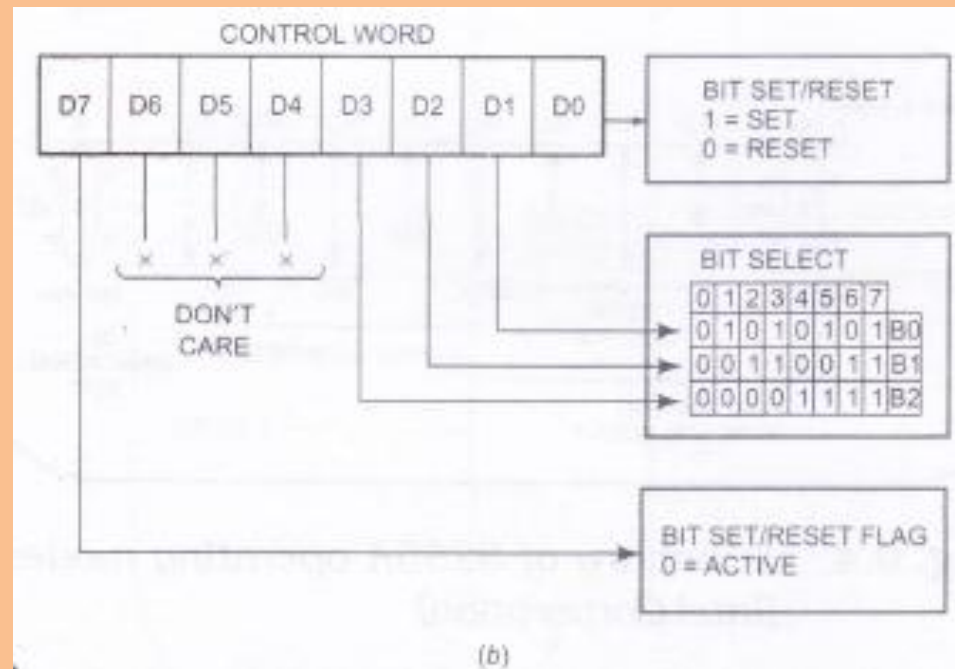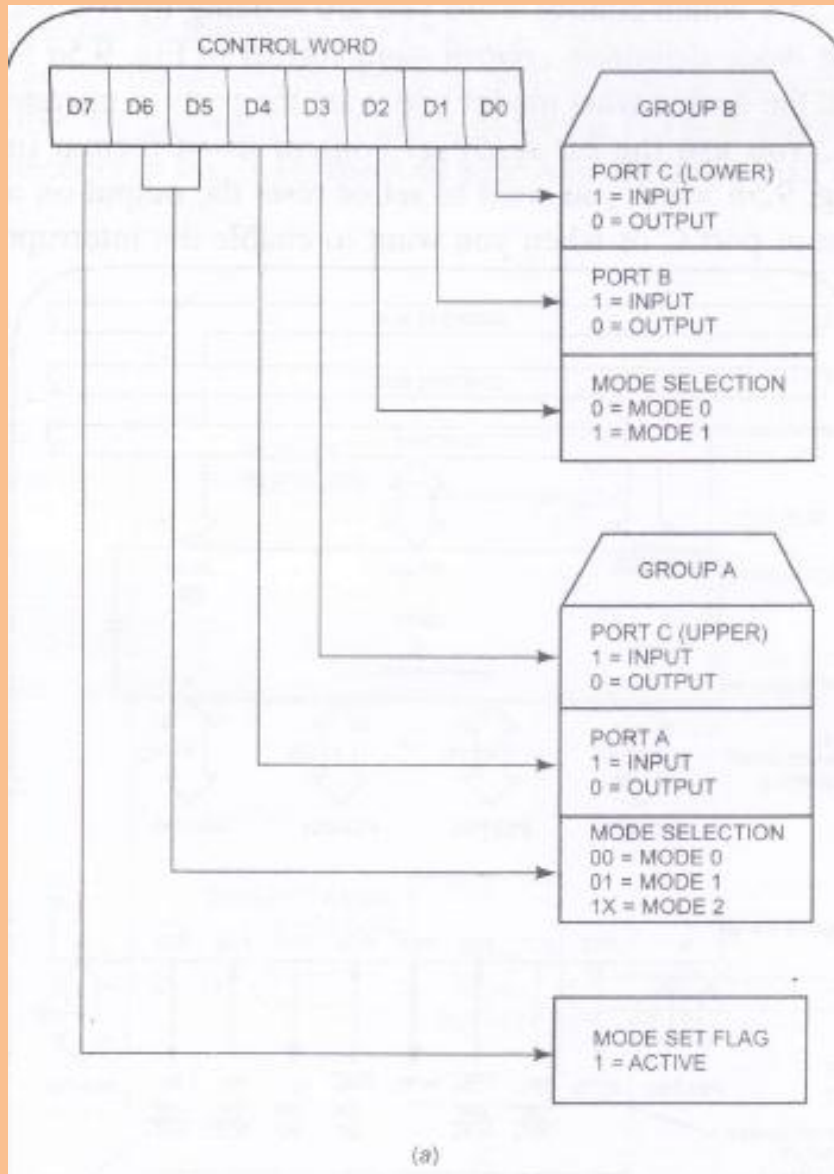


**Fig. 9.5** 8255A control word formats, (a) Mode-set control word, (b) Port C bit set/reset control word.

# Sending Control words

## ❑ *Coding:*

- MOV AL, 10001110B ;Load control word.  
MOV DX, FFFEh ;Load control register.  
OUT DX, AL
- Procedure is similar for sending both control word.

# 8255A Handshake Application Examples

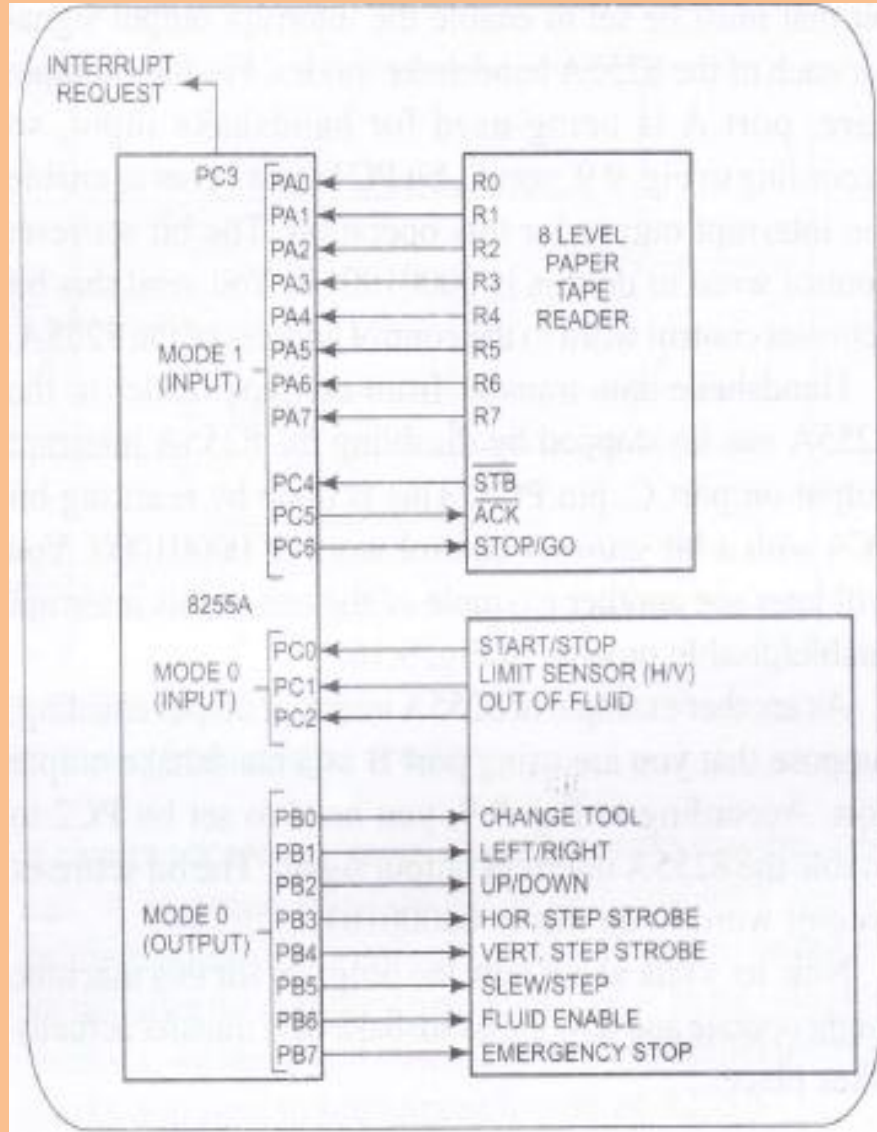

- Port A needs to be initialized for handshake input (mode1) because instruction codes have to be read in from the tape reader on a handshake basis.
- Port B needs to be initialized for simple output (mode 0).
- Port C, bits PC0, PC1 and PC2 are used for simple input of sensor signals from the lathe.
- Port C bits PC3, PC4, and PC5 function as the handshake signals for the data transfer from the tape reader connected to port A.
- Port C, bit PC6 is used for output of the STOP/GO signal to the tape reader.
- Port C, bit PC7 is not used for this example.


# Data reading from tape recorder

- Tape recorder sends data to port A of 8255.
- Tape recorder also sends  $\overline{STB}$  signal to 8255 to tell that *a new data is sent*.
- 8255 responds with IBF (Input Buffer Full) signal to be high to tell *8255 is ready for data*.
- When IBF is high  $\overline{STB}$  is high again. It causes two effects on 8255.
- 1<sup>st</sup>: 8255 latches data and tape can remove it and load new one.
- 2<sup>nd</sup>: Enables interrupt of 8086 by PC3 of 8255.

# Data reading from tape recorder

- Microprocessor are ready to read data.
- $\overline{RD}$  goes low and read from port A.
- 8255 automatically reset interrupt signal so that the second interrupt cannot cause the same data transfer.
- When RD goes high, IBF (PC5) will low again automatically by 8255, which indicate that the data transfer is complete.


# Timing Diagram

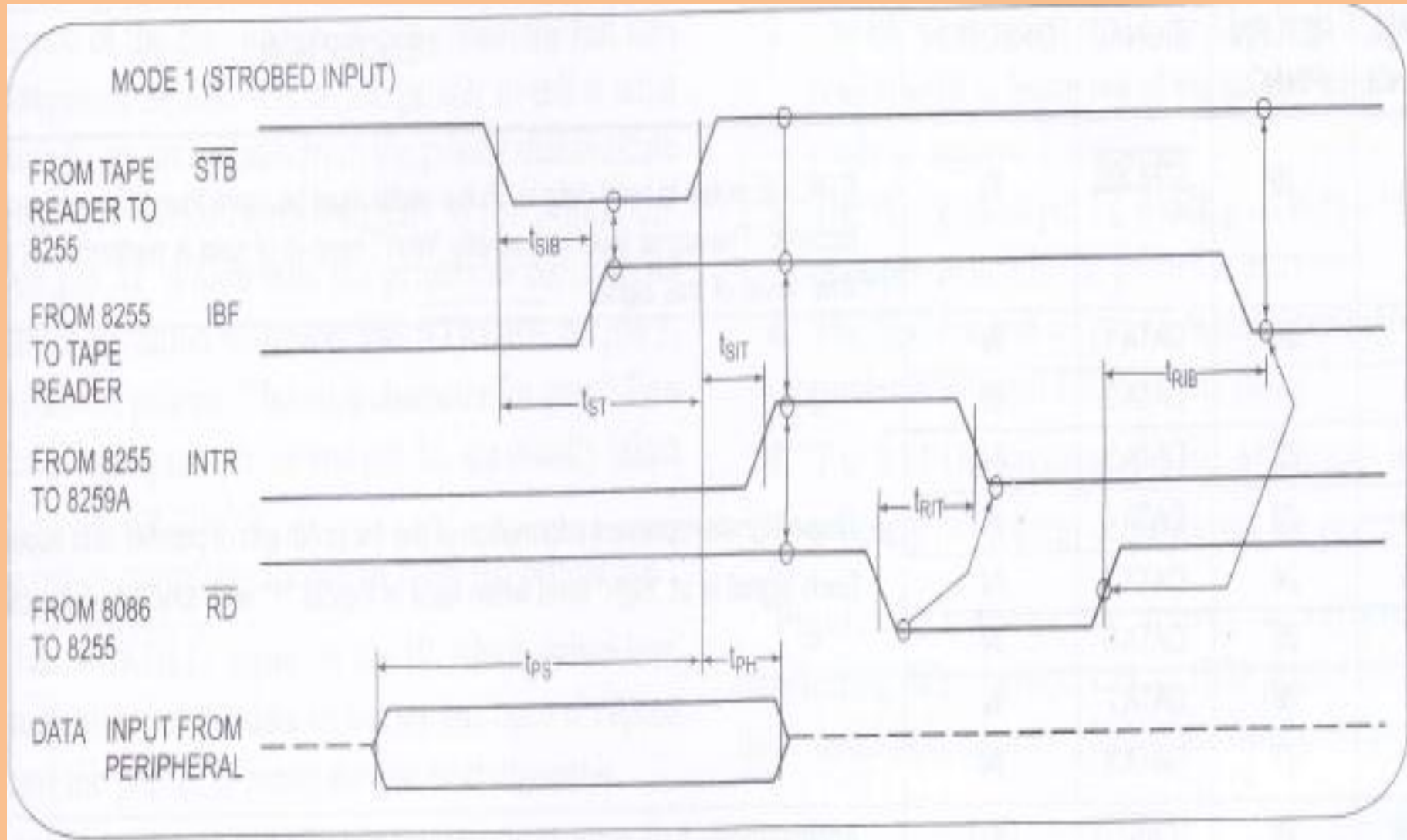

# Interfacing a Microprocessor to Keyboards
 
## □ Keyboard Types

- Mechanical Key switches
- Membrane Key switches
- Capacitive Key switches
- Hall Effect Key switches






# Interfacing a Microprocessor to Keyboards

## □ Keyboard Circuit Connections and Interfacing

- In most keyboards, the key switches are connected in a matrix of rows and columns
- Getting meaningful data from a keyboard requires the following three major tasks:
  - ✓ 1. Detect a key Press.
  - ✓ 2. Debounce the key Press.
  - ✓ 3. Encode the key press (produce a standard code for the Pressed key).



# Software Key board Interfacing

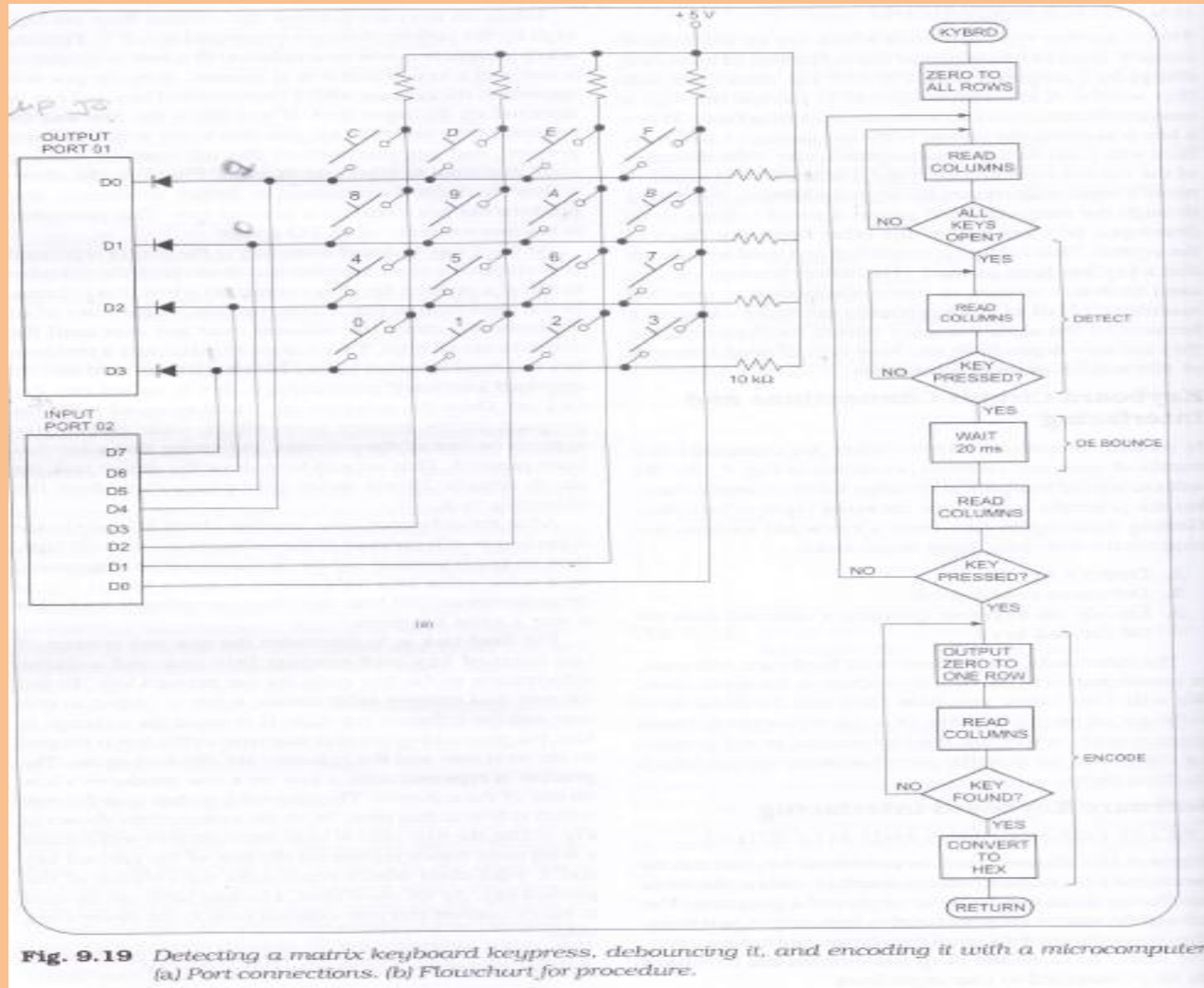

**Fig. 9.19** Detecting a matrix keyboard keypress, debouncing it, and encoding it with a microcomputer  
(a) Port connections. (b) Flowchart for procedure.


# Keyboard Interfacing with Hardware

- For systems where the CPU is too busy in other major tasks in software, an external device is used to do them.
- One example of a MOS device, which can do this is the General Instrument AY5-2376,
- The AY5 -2376 independently detects a key press by cycling a low down through the rows and checking the columns just as we did in software.
- The AY5-2376 has a feature called two-key rollover.
- This means that if two keys are pressed at nearly the same time, each key will be detected, debounced, and converted to ASCII.

# Dedicated Microprocessor Keyboard Encoders

- The 8048 microprocessor used here contains an 8-bit CPU, a ROM, some RAM, three ports and a programmable timer/counter.
- A program stored in the on-chip ROM performs the three keyboard tasks and sends the code for a pressed key out to the computer.
- The key code is sent out in serial form rather than in parallel form.
- One of the major advantages of using a dedicated microprocessor to do the three keyboard tasks is programmability.
- Special-function keys on the keyboard can be programmed to send out any code desired for a particular application.



# Dedicated Microprocessor Keyboard Encoders

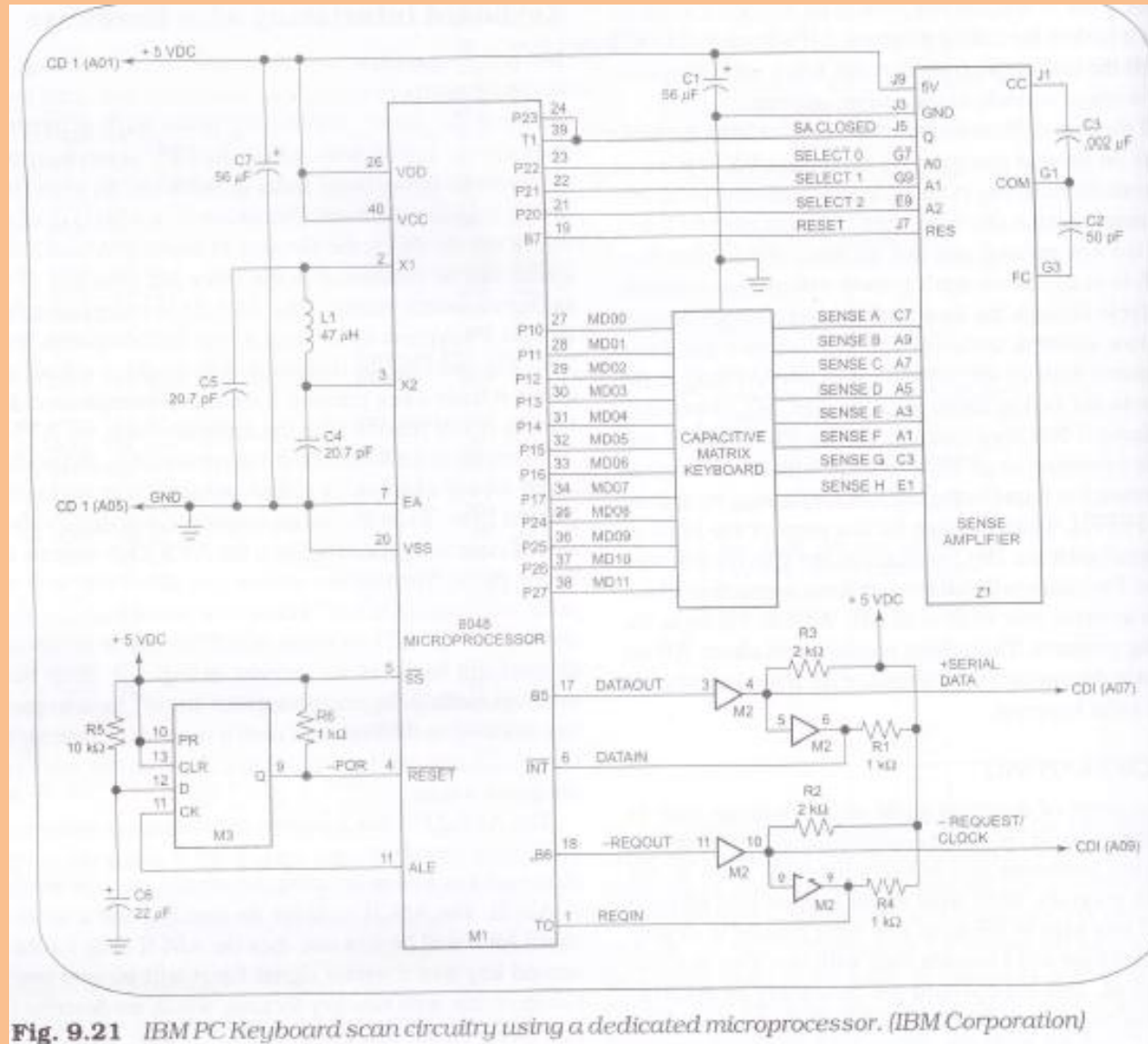


**Fig. 9.21** IBM PC Keyboard scan circuitry using a dedicated microprocessor. (IBM Corporation)
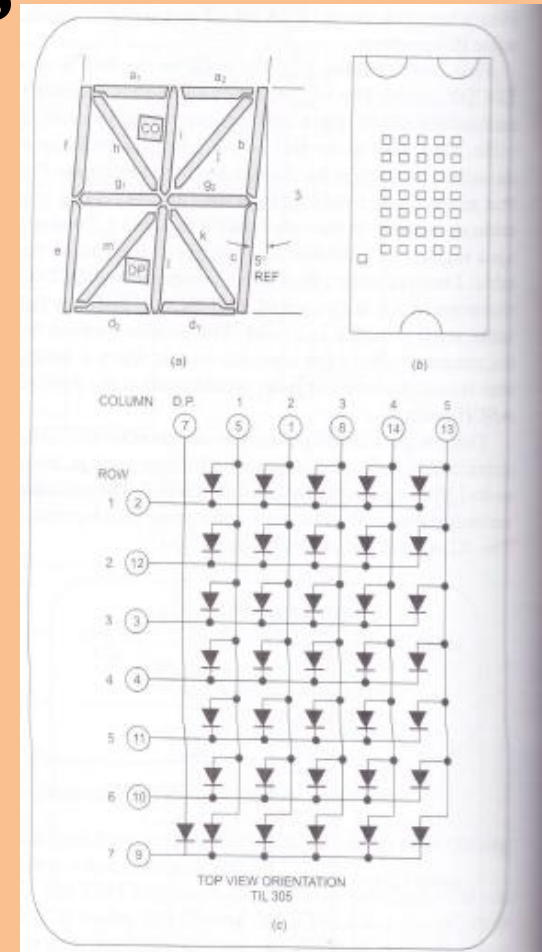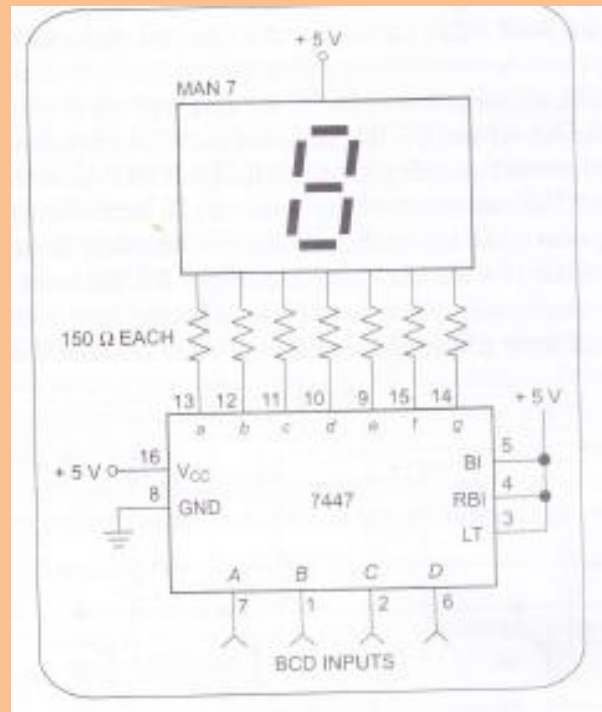
# Interfacing LED Displays to Microcomputers

- Figure shows a circuit that you might connect to a parallel port on a microcomputer to drive a single 7-segment, common-anode display.



# Software-multiplexed Led Displays

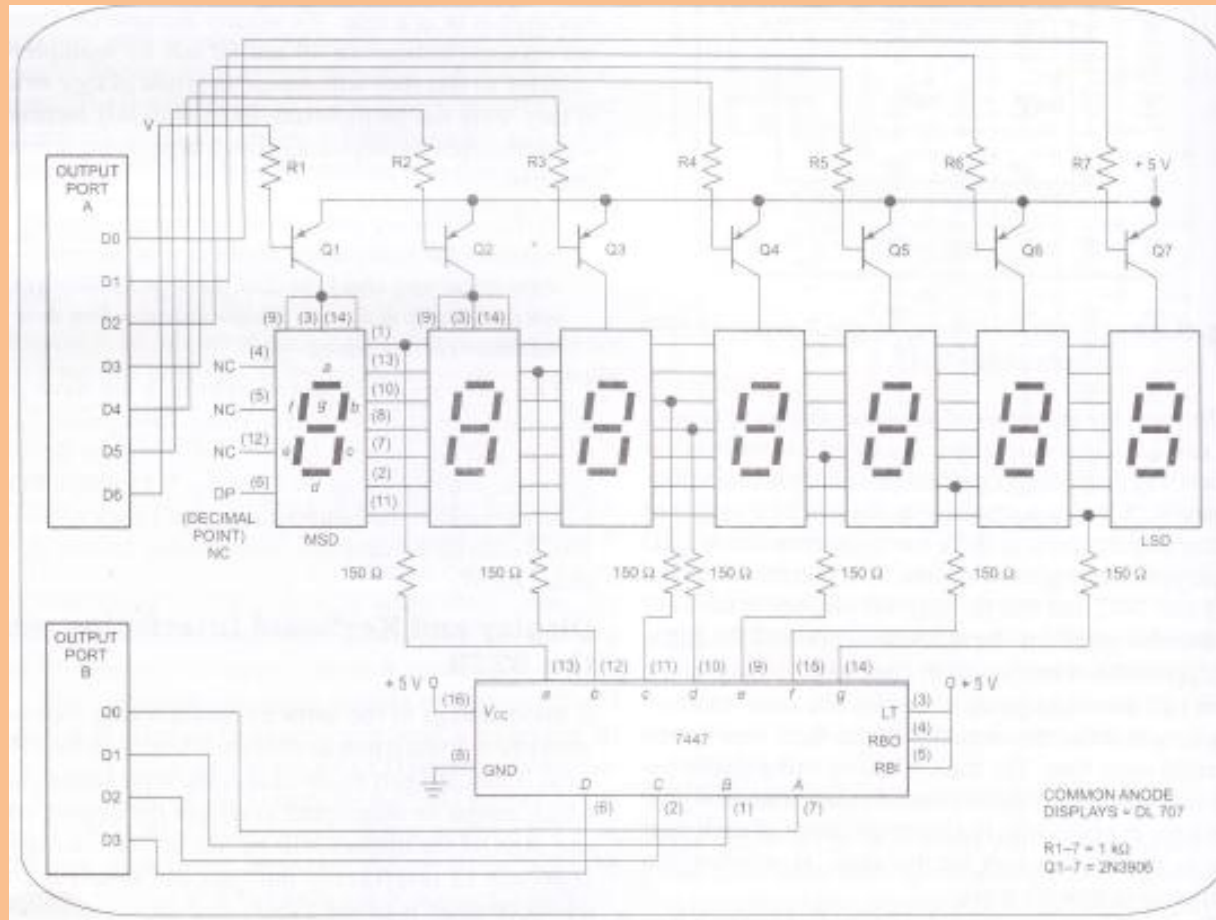


- The immediately obvious advantages of multiplexing the displays are that only one 7447 is required, and only one digit is lit at a time

# Liquid-Crystal Display Interfacing.

- Figure 9.34 shows how an Intersil ICM7211M can be connected to drive a -digit, non - multiplexed, 7-segment LCD display.
- To display a character on one of the digits, you simply put the 4-bit hex code for that digit in the lower 4 bits of the AL register and output it to the system address that digit.
- The ICM7211M converts the 4-bit hex code  $r$  to the required 7-segment code.



# Liquid-Crystal Display Interfacing.

 

**Fig. 9.34** Circuit for interfacing four LCD digits to an SDK-86 bus using Intersil ICM7211M.



# CHAPTER



# ENDS